

## Solution Products



TISP8200HDMR-S



TISP8201HDMR-S



B1250T

## Design Kit



PN-DESIGNKIT 7

# RJ11 SLIC Protection

## GR-1089-CORE Dual Supply Voltage

### Objective

The SLIC telephone interface supplies battery power, provides dialtone, and generates ringing voltage. This solution protects dual supply voltage SLIC interfaces against surge and power contact threats.

### Solution

1 Thyristor: TISP8200HDMR-S  
1 Thyristor: TISP8201HDMR-S  
2 Telecom Fuses: B1250T

### Compliance

GR-1089-CORE, Section 4, Port Types 1, 3, 5


### Alternate Recommendations

Other PortNote® Solutions:

- RJ11 SLIC Protection: GR-1089-CORE Negative Voltage Tracking
- RJ11 SLIC Protection: ITU-T Negative Voltage Tracking
- RJ11 SLIC Protection: ITU-T Dual Supply Voltage
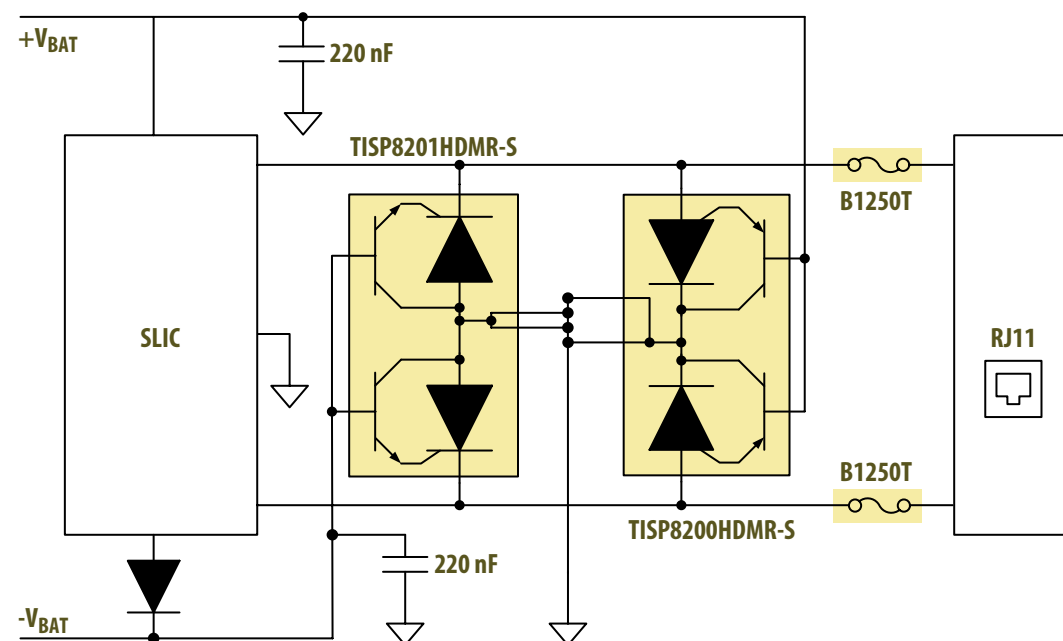
### Benefit

This solution provides a high level of protection in a small amount of PCB area.



The schematic above illustrates the application protection and does not constitute the complete circuit design. Customers should verify actual device performance in their specific applications.

# AMEYA360

## Components Supply Platform

Authorized Distribution Brand :



Website :

Welcome to visit [www.ameya360.com](http://www.ameya360.com)

Contact Us :

➤ Address :

401 Building No.5, JiuGe Business Center, Lane 2301, Yishan Rd  
Minhang District, Shanghai , China

➤ Sales :

Direct +86 (21) 6401-6692

Email [amall@ameya360.com](mailto:amall@ameya360.com)

QQ 800077892

Skype ameyasales1 ameyasales2

➤ Customer Service :

Email [service@ameya360.com](mailto:service@ameya360.com)

➤ Partnership :

Tel +86 (21) 64016692-8333

Email [mkt@ameya360.com](mailto:mkt@ameya360.com)