



Ultra Low Profile 1608 Balun 50Ω to 50Ω Balanced

Description

The BD0205F5050AHF is a low profile sub-miniature balanced to unbalanced transformer designed for differential input locations on data conversion devices such as A to D and D to A converters. In an easy to use surface mount package covering 75 MHz to 1000 MHz and with CMRR performances over 2x that of the incumbent wire wound products, this transformer is optimized to offer improved SFDR management during operation of the data converter device. The BD0205F5050AHF is ideal for high volume manufacturing and is higher performance and smaller form factor than traditional wire wound transformers. The BD0205F5050AHF has an unbalanced port impedance of 50Ω and a 50Ω balanced port impedance. This transformation enables single ended signals to be applied to differential ports on the data converter devices. The output ports have equal amplitude (-3dB) with 180 degree phase differential. The BD0205F5050AHF is available on tape and reel for pick and place high volume manufacturing.

Detailed Electrical Specifications: Specifications subject to change without notice.


Features:

- 70 1000 MHz (IL 3dB BW)
- 200-500 MHz (IL 1dB BW)
- 0.83 mm Height Profile
- 50 Ohm to 2 x 25 Ohm
- Excellent CMRR (36dB typical)
- Input to Output DC Isolation
- Surface Mountable
- Tape & Reel
- Non-conductive Top Surface
- RoHS Compliant
- Halogen Free

	ROOM (25°C)						
Parameter	Min.	Тур.	Max	Min.	Тур.	Max	Unit
Frequency	70		1000	200		500	MHz
Unbalanced Port Impedance		50			50		Ohm
Balanced Port Impedance		50			50		Ohm
Return Loss	4	4.6		11	13		dB
Insertion Loss*		3.0	3.4		0.9	1.1	dB
Amplitude Balance		0.2	0.6		0.2	0.6	dB
Phase Balance		1	3		1	3	Degrees
CMRR		36			36		dB
Power Handling			2			2	Watts
Operating Temperature	-55		+85	-55		+85	°C

^{*} Insertion Loss stated at room temperature (Insertion Loss is approximately 0.1 dB higher at +85 °C)

Outline Drawing

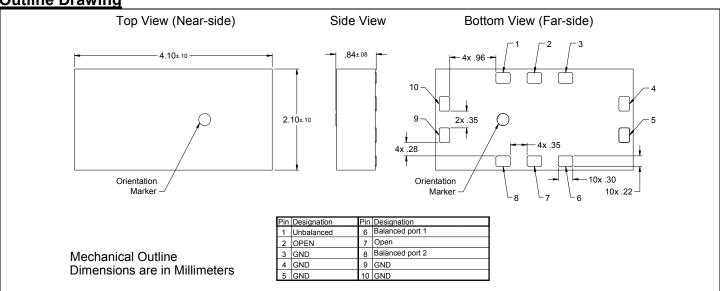




Visit us at www.anaren.com


USA/Canada: (315) 432-8909 Toll Free: (800) 411-6596 Europe: +44 2392-232392 Asia: +86 512-62749282







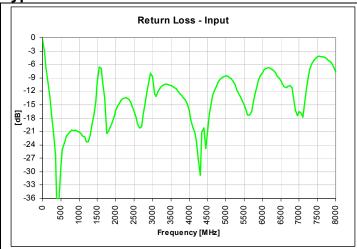
Typical Broadband Performance: 0 - 8.0 GHz.



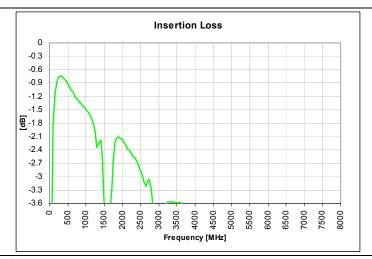

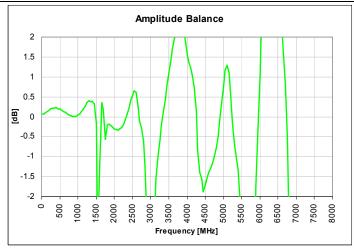

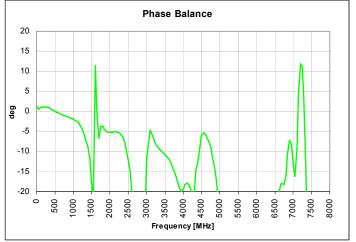

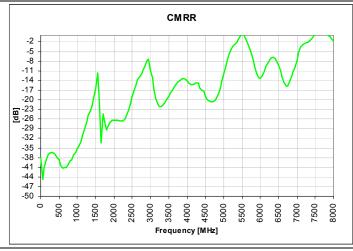




USA/Canada: (315) 432-8909 Toll Free: (800) 411-6596 Europe: +44 2392-232392 Asia: +86 512-62749282











Typical Performance: 0 MHz. to 1000 MHz.

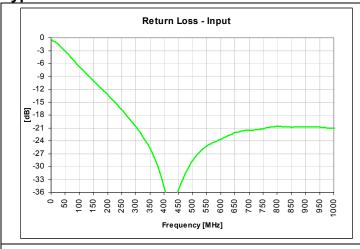

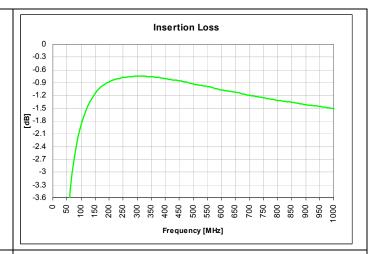

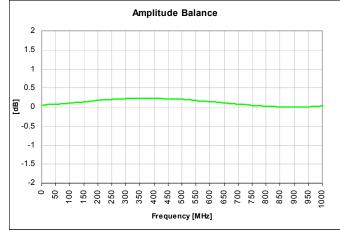

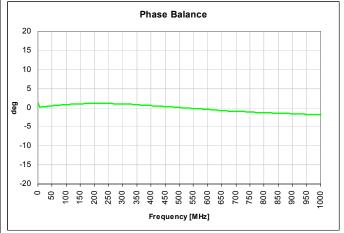

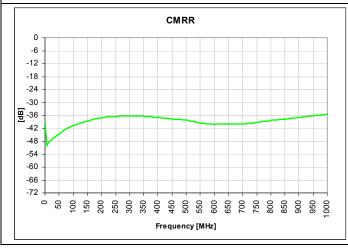



USA/Canada: (315) 432-8909 Toll Free: (800) 411-6596 Europe: +44 2392-232392 Asia: +86 512-62749282






Application in ADC Frontend:

Modern Analog-to-Digital Converter (ADC) system often uses differential architecture to suppress the even-order harmonics. The performance of ADC system is heavily influenced by amplitude and phase imbalances arising from the ADC frontend, especially in high frequency applications. Anaren's multi-layer balun BD0205F5050AHF offers superb amplitude and phase balance performance over wide frequency range, translating to excellent SFDR performance of the ADC system. BD0205F5050AHF is a ferrite free design eliminating related inter-modulation and other non-linear effects. BD0205F5050AHF provides wideband impedance match, resulting in improvement of gain flatness at high frequencies, which in turn reduces input drive requirement. Anaren's highly repeatable manufacturing process results in little part to part variation, ensuring consistent performance in production.

The schematic of a typical ADC front end application is shown below. In conjunction with many high speed ADC ICs, a bandwidth of 70MHz to 250MHz can be obtained for -1dB ripple of gain flatness. Differential load R1 and R2 are 33 ohm, slightly higher than the theoretical 25 ohm, to increase the voltage gain and reduce the required input drive, while keeping acceptable return loss. Optional series resistors, R5, R6, R7 and R8 are used to limit the amount of charge injection from the unbuffered ADC back into the analog input. Optional RC circuits, R3, R4, C4 and C5 further improve SDFR in many circumstances by supplying an additional current path to neutralize the charge injection.

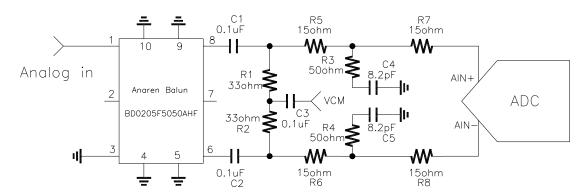

Typical ADC frontend schematic using BD0205F5050AHF



USA/Canada: (315) 432-8909 Toll Free: (800) 411-6596 Europe: +44 2392-232392 Asia: +86 512-62749282

www.anaren.com

Visit us at




Model BD0205F5050AHF

Mounting Configuration:

In order for Xinger surface mount components to work optimally, the proper impedance transmission lines must be used to connect to the RF ports. If this condition is not satisfied, insertion loss, Isolation and VSWR may not meet published specifications.

All of the Xinger components are constructed from organic PTFE based composites which possess excellent electrical and mechanical stability. Xinger components are compliant to a variety of ROHS and Green standards and ready for Pb-free soldering processes. Pads are Gold plated with a Nickel barrier.

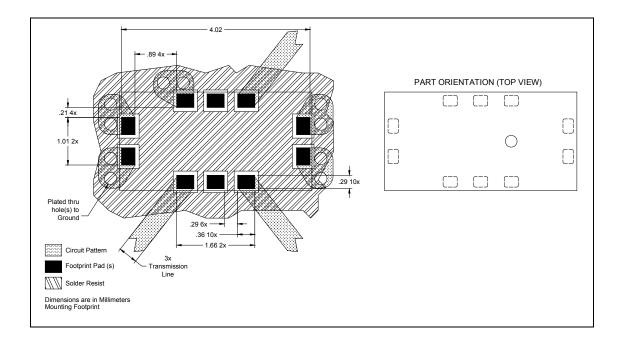An example of the PCB footprint used in the testing of these parts is shown below. In specific designs, the transmission line widths need to be adjusted to the unique dielectric coefficients and thicknesses as well as varying pick and place equipment tolerances.



Visit us at



USA/Canada: (315) 432-8909 Toll Free: (800) 411-6596 Europe: +44 2392-232392 www.anaren.com

Asia: +86 512-62749282

AMEYA360 Components Supply Platform

Authorized Distribution Brand:

























Website:

Welcome to visit www.ameya360.com

Contact Us:

> Address:

401 Building No.5, JiuGe Business Center, Lane 2301, Yishan Rd Minhang District, Shanghai , China

> Sales:

Direct +86 (21) 6401-6692

Email amall@ameya360.com

QQ 800077892

Skype ameyasales1 ameyasales2

Customer Service :

Email service@ameya360.com

Partnership :

Tel +86 (21) 64016692-8333

Email mkt@ameya360.com